

Electronic Circuits

Project

Michał Sutowicz

Kacper Jastrzębski

Date: 20-03-2023

Contents

1	Introduction	2
2	DC Analysis	2
2.1	Calculations	2
2.2	Simulations	2

1 Introduction

Assigned values:

U_{outmax} [V]	f_L [Hz]	f_H [kHz]	R_L [k Ω]	R_g [k Ω]	k_{uef}
3	20	100	2	10	40

2 DC Analysis

To perform a DC analysis, we started from manual calculations and assumed followed values:

U_{CEsat} [V]	V_{cc} [V]	I_d
1	12	$10 \times I_{B1Q}$

2.1 Calculations

2.2 Simulations